

1.Arduino UNO-Transmitter

Joystick pin	UNO pin
VCC	5V
GND	GND
VRx/X	A0
VRy/Y	A1
SW	Not connected

NRF24L01	UNO
VCC	3.3V
GND	GND
CE	D9
CSN	D10
SCK	D13
MOSI	D11
MISO	D12
IRQ	Not Connected

2. Arduino Mega — Receiver

NRF24L01	Mega2560
VCC	3.3V
GND	GND
CE	D48
CSN	D49
SCK	D52
MOSI	D51
MISO	D50
IRQ	Not Connected

LEFT IBT-2 → Mega

IBT-2 pin	Mega
RPWM	D5
LPWM	D6
R_EN	D7
L_EN	D7
VCC	5V
GND	GND

R_IS	Not connected
L_IS	Not connected

RIGHT IBT-2 → Mega

IBT-2 pin	Mega
RPWM	D8
LPWM	D9
R_EN	D10
L_EN	D10
VCC	5V
GND	GND
R_IS	Not Connected
L_IS	Not Connected

Left Motor-Left IBT-2

Left IBT-2 Terminal	Connections
B+	Battery +
B-	Battery -
M+	Left Motor-wire 1
M-	Left Motor- wire 2

Right Motor-Right IBT-2

Right IBT-2 Terminal	Connections
B+	Battery +
B-	Battery -
M+	Right Motor- wire 1
M-	Right Motor- wire 2

OLED-Mega

OLED	Mega
VDD	5V
GND	GND
SCK	D21
SDA	D20